



Upload a List of Electronic Parts to our FREE BoM Tool

Upload File

Search ...


TRENDING: 4K LIBRE COMPUTER S905X SBC SOC

Home / Blog / SEPIC Converter Based On MT3608 Is Open Source


1200 x 125 AD

TOP PCB Companies



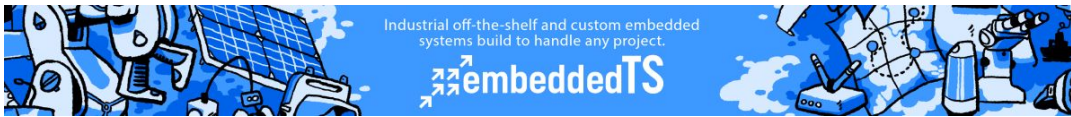

874 x 90 AD

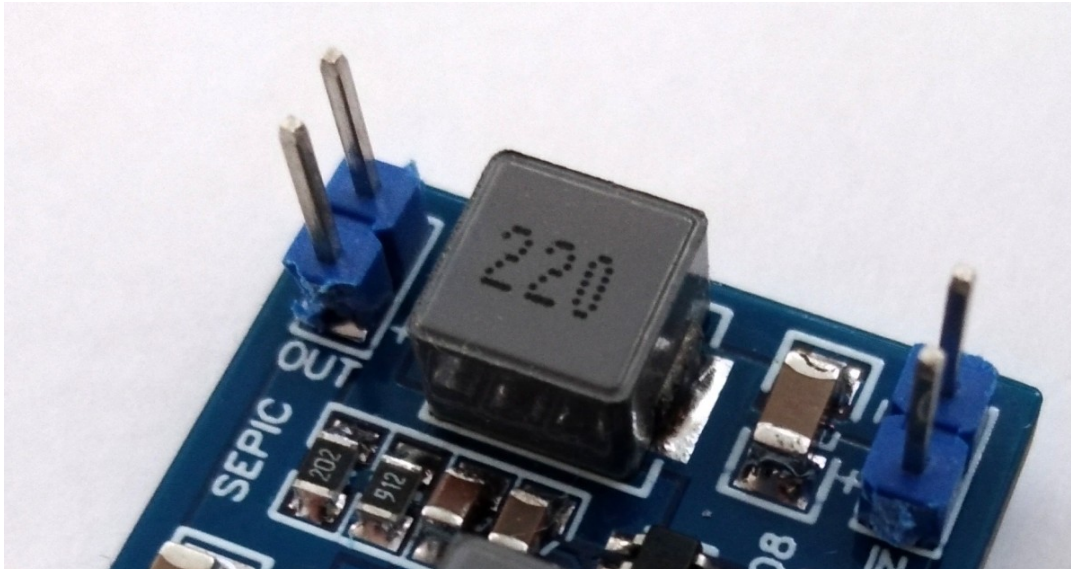

POWER SUPPLY

## SEPIC CONVERTER BASED ON MT3608 IS OPEN SOURCE

27 May, 2021

3.310 Views

2 Comments

DC-DC converters are needed in almost every commercial product, whether it is industrial, medical, defensive, automotive, or any other application. These converters are electronic circuits that can convert the DC voltage from one level to another. There are two types of DC-DC converters: linear and switching converters. Linear converters are resistive which means that they use resistive voltage drop to create a regulated output voltage. This also means that the input voltage should always be higher than the input voltage, and linear converters can only step down a voltage level. On the other hand, switching converters perform the conversion by storing the energy periodically in the energy storage elements like capacitors and inductors. The stored energy is then provided to the load at the desired voltage level.

There are several benefits of switching converters. Firstly, switching converters are highly efficient. They have an efficiency in the range of **80-90%**. Moreover, the buck-boost converters can step up and down the voltage levels to maintain the output voltage. Additionally, thermal management is simplified due to lower losses.

Get New Posts By Email:

Enter your email

Subscribe

CATEGORIES

BLOGROLL

Get New Posts By Email:

Enter your email

Subscribe

Join 97,426 other subscribers



Newsletter

Subscribe

ARCHIVES

Select Month

TAGCLOUD

Aaeon AI Arduino

Battery BLE Bluetooth camera

DC-DC display ESP32

ESP8266 FPGA GPS I2C IoT

Kickstarter LCD Led Linux Mcu

MEMS Microchip Microcontroller

MOSFET Motor OLED Oscilloscope

PCB Power supply PWM

Raspberry Pi regulator RISC-V


SBC Sensor SOC SOM

STMicroelectronics Switch Switching

temperature Texas Instruments TFT

USB Wifi


Subscribe to Our RSS Feed

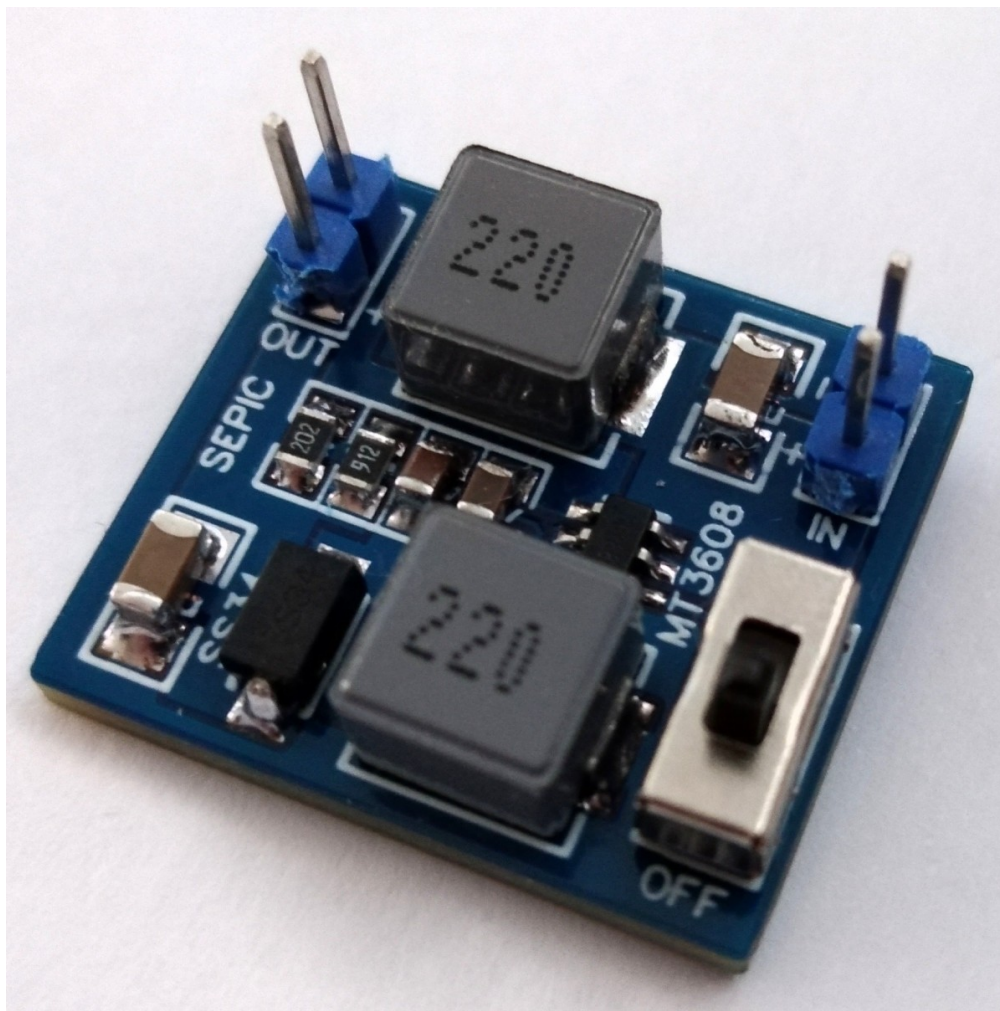

TOP PCB Companies
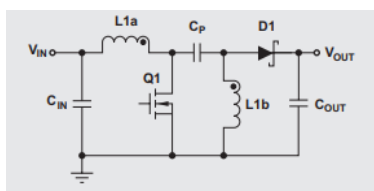
## SEPIC

SEPIC (Single Ended Primary Inductor Converter) type of converter is very similar to the traditional buck-boost converters. SEPIC can step up as well as step down the voltages accordingly. The simple buck-boost converters consist of two MOSFETs used as switches. SEPIC converters, however, are characterized using two inductors, one of them is at the input that is for coupling, and another one is connected to the ground.



Source: <https://www.ti.com/lit/an/slyt309/slyt309.pdf>


The SEPIC topology consists of an input capacitor, an output capacitor, coupled inductors, a diode, and a power MOSFET. To understand the working of the SEPIC, let's assume that the switch is first open. In this state, it can be easily seen that the input capacitor  $C_{IN}$  is charged at the input voltage. The voltage across the inductor  $L1b$  must be the same as  $V_{OUT}$  and therefore, the voltage across the switch must be  $V_{OUT} + V_{IN}$ .

When the switch is closed, the capacitor  $C_P$  is charged to the input voltage which then charges  $L1b$ . Energy is also stored in the inductor  $L1a$  from the input during this state. When the switch is opened again, the inductor  $L1a$  discharges to the output capacitor via diode and power the load.

The converter's output voltage can be controlled by adjusting the duty cycle of the MOSFET. SEPICs are mostly controlled by PWM regulator ICs and a microcontroller that drives the gate of the MOSFET according to the sensed voltages. But for compact devices, DC-DC converter ICs are widely used. They consist of integrated MOSFETs, an internal voltage reference for feedback, and are highly efficient.

SEPIC PCB Based On MT3608

Stefan Wagner from Germany designed a SEPIC PCB based on MT3608 DC-DC converter IC. MT3608 is a very compact boost converter IC that provides up to **97% efficiency** and also allows a wide input voltage range. In addition, MT3608 includes under-voltage lockout, current limiting, and thermal overload protection to prevent damage in the event of an output overload. The schematic of the SEPIC design is as follows:

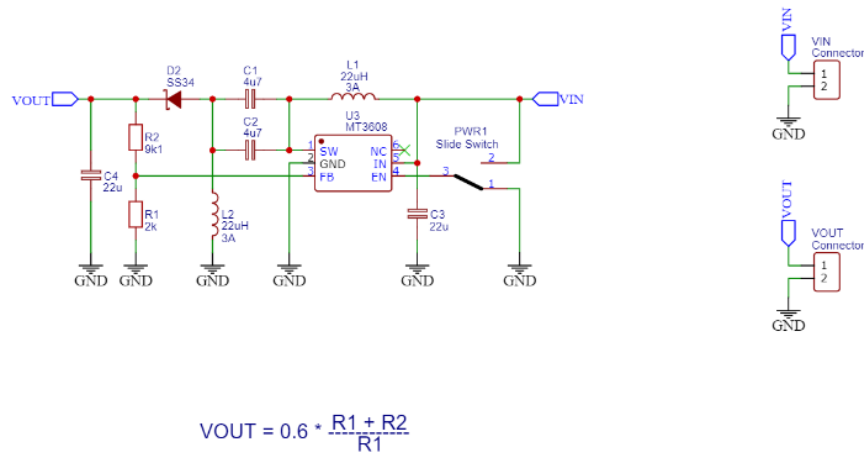

$$VOUT = 0.6 \cdot \frac{R1 + R2}{R1}$$

Source: [https://github.com/wagiminotor/Power-Boards/blob/master/SEPIC\\_MT3608/SEPIC\\_MT3608\\_schematic.pdf](https://github.com/wagiminotor/Power-Boards/blob/master/SEPIC_MT3608/SEPIC_MT3608_schematic.pdf)

The output voltage is divided by a resistive voltage divider to the FB pin of the IC. The voltage at the FB pin is compared to an internal reference voltage of 0.6V, and the PWM is controlled accordingly.

The complete project including the Gerber files, performance results and BOM can be found at [https://github.com/wagiminotor/Power-Boards/tree/master/SEPIC\\_MT3608](https://github.com/wagiminotor/Power-Boards/tree/master/SEPIC_MT3608)

Please follow and like us: [Follow](#) [Share](#) [Tweet](#) [Save](#)

TAGS

- BUCK-BOOST
- DC-DC CONVERTERS
- EFFICIENCY
- MT3608
- POWER CONVERTERS
- SEPIC
- VOLTAGE REGULATORS


RELATED POSTS



13 August, 2019  
AI@EDGE COMPACT FANLESS EMBEDDED BOX PC WITH NVIDIA JETSON TX2 AND 4 POE LAN



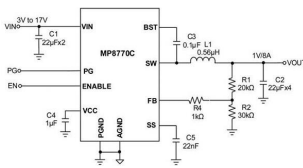24 July, 2019  
LATEST SOLUTIONS FROM CUI & DIGI-KEY BY OEMSECRETS.COM



8 May, 2021  
MPS' MP8770C IS A 3 V TO 17 V, 8 A, SYNCHRONOUS STEP-DOWN CONVERTER WITH FORCED CCM



About DM  
Email : [electronicslab45@gmail.com](mailto:electronicslab45@gmail.com)

[VIEW ALL POSTS BY DARSHIL](#)

Subscribe

Connect with

Facebook

Twitter

Google

Reddit

Login

guest

Join the discussion

B

I

U

Link

List

Quote

Code

Image

More

2 COMMENTS

⚡

🔥

Bret Tschacher

2 years ago

I think it's cool that DC/DC converters are being developed and this is an example of how things are getting smaller, with lower component count, which obviously requires less raw material, up to a point of being able to handle specific loads. It's like re inventing a wheel, sort of. With that, many loads require such a low level of power to accomplish tasks. But there are still those tasks that require a bit more power. The 97% rating impresses me, I can't wait to see 100+ %, that's a joke as I'm sure we can all understand. Perpetual energy impresses me even more!

+ 0

Reply

David

2 years ago

SEPIC converters are your friend in battery powered applications. For example, a SEPIC converter is useful when you need to get 3.3VDC from a single-series (1S) Li-Ion or Li-Polymer cell who's output can range from a bit less than 3V to 4.2V. One advantage the SEPIC topology has over both Buck-Boost and Ćuk topologies is that its output is non-inverting. [1] Another is that the series (flying) capacitor provides some input/output DC isolation.[1] And finally in both SEPIC and Ćuk topologies the two inductors can be coupled which results in using one part instead of two, plus the inductance value needed is lower compared to using two separate inductors.[2] For example the required inductance is halved when both inductors share the same core.[3] Note, the SEPIC converter example in this post does not use coupled inductors.

\* References:

1. Switch Mode Power Supply Topologies Compared

[https://www.we-online.com/web/en/electronic\\_components/news\\_pbs/blog\\_pbcm/blog\\_detail-worldofelectronics\\_45887.php](https://www.we-online.com/web/en/electronic_components/news_pbs/blog_pbcm/blog_detail-worldofelectronics_45887.php)

2. Benefits of a coupled-inductor SEPIC converter

<https://www.ti.com/lit/an/slyt411/slyt411.pdf>

3. Selecting Coupled Inductors for SEPIC Applications

[https://www.coilcraft.com/getmedia/adce25eb-776e-44d2-950e-32e937d63a86/doc639\\_Selecting\\_SEPIC\\_Inductors.pdf](https://www.coilcraft.com/getmedia/adce25eb-776e-44d2-950e-32e937d63a86/doc639_Selecting_SEPIC_Inductors.pdf)

+ 1

Reply

we-online.com

World of Electronics

Facebook

Twitter

Instagram

LinkedIn

Reddit

Menu

Community

Blog

Downloads

Articles

Links

Projects

Audio

MCU Development

Miscellaneous

Power

Oscillators – Timers

Arduino & Raspberry

Microcontroller

Motor Control

Light – Power Control

Sensors – Detectors

Connect With Us

Facebook

Twitter

LinkedIn

Contact Us

Work For Us

https://www.electronics-lab.com/sepic-converter-based-on-mt3608-is-open-source/

5/6

TOP PCB Companies

[email@domain.com](#)

[submit](#)

© ELECTRONICS-LAB.COM – 2023, WORK IS LICENCED UNDER CC BY SA 4.0



[PRIVACY POLICY](#)   [TERMS OF SERVICE](#)   [USER AGREEMENT](#)

TOP PCB Companies

