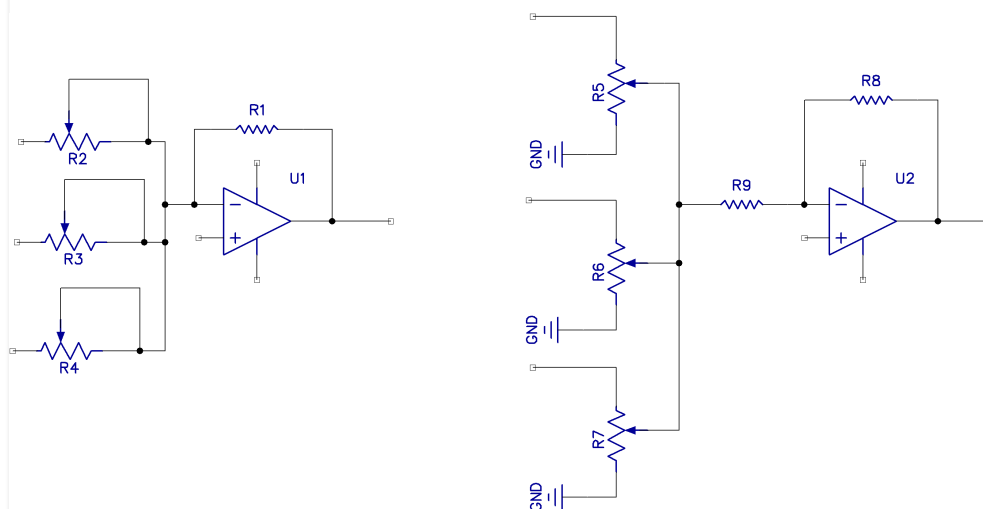




HOW TO BUILD AN AUDIO MIXER

Posted by Graham Lambert | DIY Electronics | 5



An audio mixer is a circuit for combining two or more analog signals so that they do not interfere with each other or cause loading on the source signals. They are mostly used to mix sound tracks from individual instruments like a microphone, guitar, and drums to create a master song track.

PCBWay

PCB Fabrication & Assembly

ONLY \$5 for 10 PCBs

✓ 24-hour Build Time ✓ Quality Guaranteed
 ✓ Most Soldermask Colors:

Order now

A [professional-level mixer](#) may have dozens of channels and settings for each channel, including presets, built-in effects, graphic equalizers, monitor controls, and output amplifiers to name a few.

But for this article, we are going to build a more simple, but still effective three channel stereo audio mixer.

MIXER DESIGNS

Get new tutorials sent to your inbox!

Circuit Basics

ULTIMATE GUIDE TO THE ARDUINO VIDEO COURSE

LEARN MORE

PCBWay

Professional

3D Printing

Start from ONLY \$5

Produces smooth, durable and accurate parts
 50+ Materials Available

Fast & Cheap

CNC Machining


Start from ONLY \$50

Machined prototypes in as fast as 1 day
 High-precision tolerances +/-0.005" - 0.01"

Get Quote Online

The basic idea behind a mixer is this: different inputs are fed into a common summing point, and these are added and then multiplied by the gain of the summing amplifier. Shown below are some input scenarios you may see on the internet. But I have avoided them for a couple of reasons.

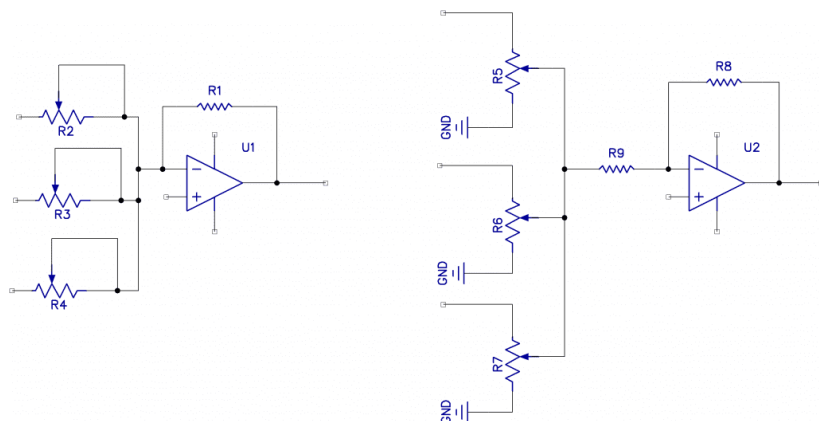
The circuit on the left will have a varying input impedance depending on the slider setting, and the circuit on the right will cause a change in level on the adjacent channels when the slider is right down low. The circuit on the right does have the advantage of dealing with extreme input levels.





OUR DESIGN

For this tutorial, we will build a mixer of our own design. Our mixer will have two stages: one input pre-amplifier per channel and an output summing amplifier. The schematic below is for a *mono* three-channel mixer with a master volume. To make this a stereo mixer, simply duplicate the circuit for the other channel. They can share the same power supply.

Here is the schematic:

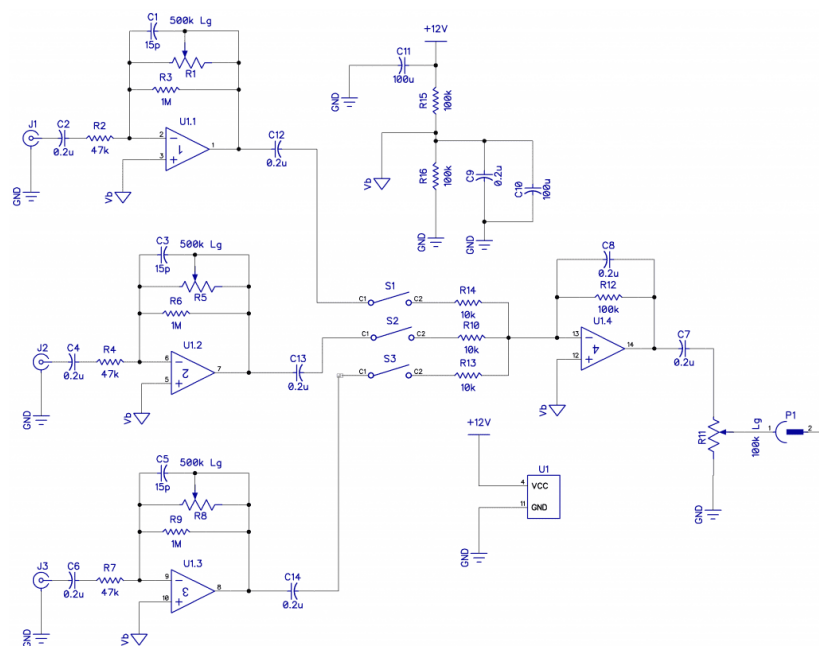

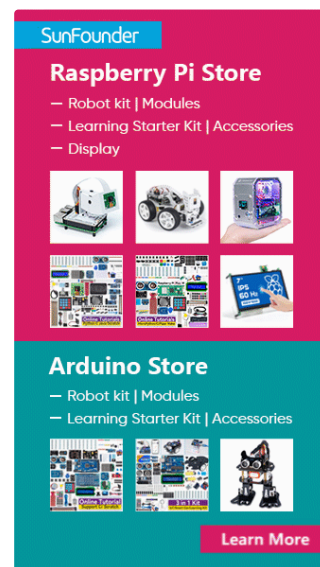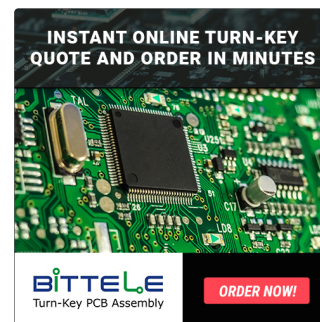We want the input impedance presented to each input to be constant and not a function of the gain setting. So here, the input impedance will be 47k to match most audio sources and dynamic microphones. There will be three



mono channels. The mixer will run on a single supply from a [12V power supply](#) (this imposes a severe constraint on the range of signal headroom).

I used a common [LM324 quad op-amp](#) (not the best for low noise and some low noise quad op-amps might be quieter, but I had some lying around). The LM324 is designed for single-supply operation and has four separate op-amps. All four op-amps used in the circuit above are from a single LM324 chip.

[1M Ohm resistors](#) R3, R6, and R9 are in parallel with the input potentiometers. The purpose of this is to keep a constant DC bias on the op-amp and prevent slider noise.

[Capacitors](#) C1, C3, and C5 tailor the upper-frequency response to 20kHz, while the input capacitors C2, C4, and C6 tailor the lower frequency response to 20Hz.

[Switches](#) S1, S2, and S3 turn the channels off.

Resistors R15 and R16 divide the supply rail in half and provide a 6V bias voltage for all the non-inverting inputs. R11 is the main volume control. Note that all potentiometers should be the [logarithmic type \(audio taper\)](#).

HOW IT WORKS

LM324 op-amps U1.1, U1.2, and U1.3 are the input pre-amplifiers. Their function is to provide a suitable input impedance to the microphones and this is set to 47k by resistors R2, R4, and R7.

Potentiometer R1 sets the gain of the input amplifier. This potentiometer sets the actual level of each input as it will be presented to the summing amplifier. Resistor R3 is only there to prevent scratchy noise as the potentiometer is adjusted.

Capacitor C1 provides a high-frequency roll-off filter to keep out radio frequency interference and inaudible signal oscillations.

After the pre-amplification step, switches S1, S2, and S3 will allow us to mute any channel.

Resistors R14, R10, and R13 are the actual mixer part. The input to U1.4 is a virtual earth, which causes the virtual voltage at this point to be the sum of all three inputs. This is amplified 10 times by U1.4 because the gain of the op-amp is defined by the ratio of R12 to any one of the input resistors. Potentiometer R11 sets the final output level before it is sent to the output jack.

The gain of the summing amplifier is expressed as $A = R12/R14$ or 10X and the output of the combined inputs is $V_{out} = -(A \cdot V1 + A \cdot V2 + A \cdot V3)$.

This can be simplified into $-A(V1 + V2 + V3)$, thus called a summing amplifier.


Note that there is a minus sign there as the op-amp is working in its inverting mode.

Hope you build this three channel stereo audio mixer! Let us know in the comments below how it works for you!




SHARE: [f](#) [t](#) [g+](#) [p](#) [e](#)


RELATED POSTS

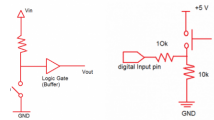


Pull-up and Pull-down Resistors

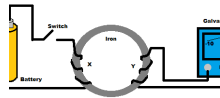

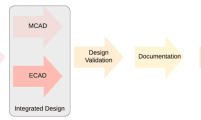A Practical Guide to Inductors and Inductance



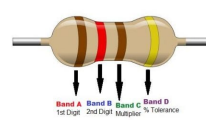The Top Five EDA/eCAD Programs for Circuit Design



How Resistors Work

5 COMMENTS

Jeff Verive on February 21, 2021 at 4:34 am

The corner frequency of the summation amp in the proposed circuit seems much too low. The 0.2uF capacitor in parallel with the 100k feedback resistor is going to create a low-pass filter that will attenuate most audio frequencies.

REPLY

ANTHONY on July 14, 2022 at 2:39 am

I agree, the $f_c(LP)$ would be 16.93 Hz. The $f_c(LP)$ should never be lower than the $f_c(HP)$ – The HP would be 20k Hz which would be correct if it were the LP (and the Pot was set to 500K). I think your resistor and cap values are backwards. Switch C1 and R1 with C2 and R2. On top of that, the location of the pot should actually be before the HP cap and resistor. If you want a band pass filter, then the cap and the resistors should be permanent (no Pot) – unless you want to adjust the band pass, in that case, you are making a preamp.

Remember $f_c(LP) = 1/(2\pi C1 * R1)$ – at least in your schematic – and it is where the frequency begins to drop off (the negative slope)
 $f_c(HP) = 1/(2\pi C2 * R2)$ and it is where the slope is positive, and noise begins to be audible.

REPLY

pb on April 28, 2022 at 5:59 pm

S1, S2, S3 should be after 10K resistors and should be two ways one side connected to the ground to mute, another to the summing opamp

REPLY

Sim on January 1, 2023 at 7:59 pm

Maybe the input signals' ground should be Vb and not GND?

REPLY

lawrence on January 14, 2023 at 11:10 pm

The input is referenced to the PS rail to give it more headroom, using Vb may introduce some clipping in some instances, although that might be ideal if you want some distortion type sound effects , which is what i'm currently looking into. Cheers.

REPLY

LEAVE A REPLY

Your email address will not be published. Required fields are marked *

COMMENT

NAME *

EMAIL *

WEBSITE

- ☐ Save my name, email, and website in this browser for the next time I comment.
- ☐ Notify me of follow-up comments by email.
- ☐ Notify me of new posts by email.

For security, use of Google's reCAPTCHA service is required which is subject to the Google [Privacy Policy](#) and [Terms of Use](#).

[I agree to these terms.](#)

POST COMMENT

Copyright **Circuit Basics**

[Raspberry Pi](#) [Arduino](#) [DIY Electronics](#) [Programming](#) [Videos](#) [Resources](#) [About](#) [Contact Us](#) [Privacy Policy](#) [!\[\]\(d3fb9f94af8b26d1c844efa9a98805b0_img.jpg\)](#) [!\[\]\(78eb1652b591ce460bbb1a853a52e223_img.jpg\)](#) [!\[\]\(73569cd2fc0daa66f7f79a4aa32515bb_img.jpg\)](#) [!\[\]\(b12ef55cf189ee2bc15774f5ac32d31a_img.jpg\)](#)

